

EE230:experiment No.5

Opamp circuits-3

Mudavtah vishnuvardhan,200070044

February 13, 2022

1 Overview of the experiment

1.1 Aim of the experiment

To simulate the following circuits using NGSPICE and compare the results with experimental observations:


1. Photodiode application circuit using op-amp LM324
2. 3 op-amp based Instrumentation Amplifier

1.2 Methods


The simulating software used is Ngspice. We used the provided model files for diode and op-amp.

2 Circuit Design

2.1 Photodiode Application Circuit

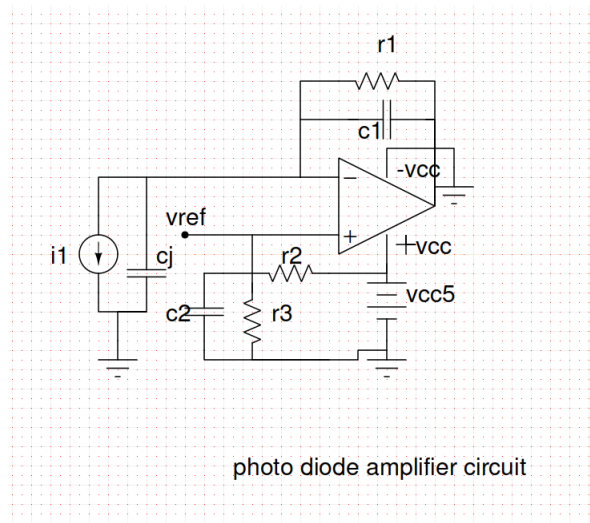

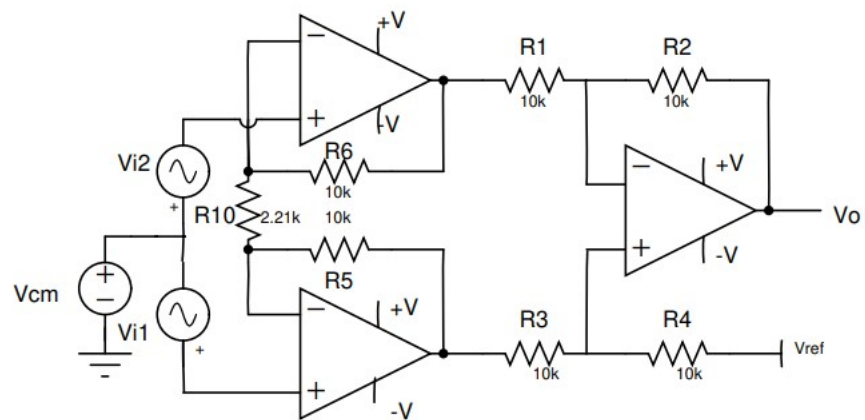2.2 3 op-amp based Instrumentation Amplifier



3 simulation results

3.1 Code Snippet

All the files which are included in the code using `.include` command are already uploaded on moodle in lab submission.

photo diode-current dc analysis

photo diode

`.SUBCKT LM324 1 2 3 4 5`

`C1 11 12 5.544E-12`

`C2 6 7 20.00E-12`

`DC 5 53 DX`

`DE 54 5 DX`

`DLP 90 91 DX`

`DLN 92 90 DX`

`DP 4 3 DX`

`EGND 99 0 POLY(2) (3,0) (4,0) 0 .5 .5`

`FB 7 99 POLY(5) VB VC VE VLP VLN 0 15.91E6 -20E6 20E6 20E6 -20E6`

`GA 6 0 11 12 125.7E-6`

`GCM 0 6 10 99 7.067E-9`

`IEE 3 10 DC 10.04E-6`

`HLIM 90 0 VLIM 1K`

`Q1 11 2 13 QX`

`Q2 12 1 14 QX`

`R2 6 9 100.0E3`

`RC1 4 11 7.957E3`

`RC2 4 12 7.957E3`

`RE1 13 10 2.773E3`

`RE2 14 10 2.773E3`

`REE 10 99 19.92E6`

`RO1 8 5 50`

`RO2 7 99 50`

`RP 3 4 30.31E3`

`VB 9 0 DC 0`

`VC 3 53 DC 2.100`

`VE 54 4 DC .6`

`VLIM 7 8 DC 0`

`VLP 91 0 DC 40`

```

VLN 0 92 DC 40
.MODEL DX D(IS=800.0E-18)
.MODEL QX PNP(IS=800.0E-18 BF=250)
.ENDS
i 0 1 dc
cj 1 0 11p
c1 1 2 3.3p
r1 1 2 1.4Meg
vref 3 0 0.1
vcc1 4 0 15v
vcc2 5 0 -15v
r2 3 4 13.7k
r3 3 0 280
c2 3 0 1u
x1 3 1 4 5 2 LM324
.dc i 0 2.4u 0.1u
.control
run
plot v(2)
.endc
.end

```

photo diode-current ac analysis

photo diode

.SUBCKT LM324 1 2 3 4 5

C1 11 12 5.544E-12

C2 6 7 20.00E-12

DC 5 53 DX

DE 54 5 DX

DLP 90 91 DX

DLN 92 90 DX

DP 4 3 DX

EGND 99 0 POLY(2) (3,0) (4,0) 0 .5 .5

FB 7 99 POLY(5) VB VC VE VLP VLN 0 15.91E6 -20E6 20E6 20E6 -20E6

GA 6 0 11 12 125.7E-6

GCM 0 6 10 99 7.067E-9

IEE 3 10 DC 10.04E-6

HLIM 90 0 VLIM 1K

Q1 11 2 13 QX

Q2 12 1 14 QX

R2 6 9 100.0E3

RC1 4 11 7.957E3

RC2 4 12 7.957E3

RE1 13 10 2.773E3

RE2 14 10 2.773E3

REE 10 99 19.92E6

RO1 8 5 50

RO2 7 99 50

RP 3 4 30.31E3

VB 9 0 DC 0

VC 3 53 DC 2.100

VE 54 4 DC .6

VLIM 7 8 DC 0

VLP 91 0 DC 40

VLN 0 92 DC 40

.MODEL DX D(IS=800.0E-18)

.MODEL QX PNP(IS=800.0E-18 BF=250)

.ENDS

```
      i 0 1 dc 1.5u ac 1
cj 1 0 11p
c1 1 2 3.3p
r1 1 2 1.4Meg
vref 3 0 0.1
vcc1 4 0 15v
vcc2 5 0 -15v
r2 3 4 13.7k
r3 3 0 280
c2 3 0 1u
x1 3 1 4 5 2 LM324
.ac dec 10 10 100Meg
.control
run
plot vdb(2)
.endc
.end
```

```

instrumentation amplifier-part a instrumentation amplifier
.subckt ua741 1 2 3 4 5
c1 11 12 8.661E-12
c2 6 7 30.00E-12
dc 5 53 dx
de 54 5 dx
dlp 90 91 dx
dln 92 90 dx
dp 4 3 dx
egnd 99 0 poly(2) (3,0) (4,0) 0 .5 .5
fb 7 99 poly(5) vb vc ve vlp vln 0 10.61E6 -10E6 10E6 10E6 -10E6
ga 6 0 11 12 188.5E-6
gcm 0 6 10 99 5.961E-9
iee 10 4 dc 15.16E-6
hlim 90 0 vlim 1K
q1 11 2 13 qx
q2 12 1 14 qx
r2 6 9 100.0E3
rc1 3 11 5.305E3
rc2 3 12 5.305E3
re1 13 10 1.836E3
re2 14 10 1.836E3
ree 10 99 13.19E6
ro1 8 5 50
ro2 7 99 100
rp 3 4 18.16E3
vb 9 0 dc 0
vc 3 53 dc 1
ve 54 4 dc 1
vlim 7 8 dc 0
vlp 91 0 dc 40
vln 0 92 dc 40
.model dx D(Is=800.0E-18 Rs=1)
.model qx NPN(Is=800.0E-18 Bf=93.75)
.ends

```

```

vcm 1 0 dc
vi1 1 2 0
vi2 1 4 0
x3 2 3 6 7 8 ua741
x2 4 5 9 10 11 ua741
r10 3 5 2.21k
r5 5 11 10k
vcc31 6 0 15v
vcc32 7 0 -15v
vcc21 9 0 15v
vcc22 10 0 -15v
r6 3 8 10k
r1 8 12 10k
r2 12 13 10k
r3 11 14 10k
r4 14 15 10k
vref 15 0 0
x1 14 12 16 17 13 ua741
vcc11 16 0 15v
vcc12 17 0 -15v
.dc vcm -2 2 1m
.control
run
plot v(13)
.endc
.end

```



```

instrumentation amplifier-part c instrumentation amplifier
.subckt ua741 1 2 3 4 5
c1 11 12 8.661E-12
c2 6 7 30.00E-12
dc 5 53 dx
de 54 5 dx
dlp 90 91 dx
dln 92 90 dx
dp 4 3 dx
egnd 99 0 poly(2) (3,0) (4,0) 0 .5 .5
fb 7 99 poly(5) vb vc ve vlp vln 0 10.61E6 -10E6 10E6 10E6 -10E6
ga 6 0 11 12 188.5E-6
gcm 0 6 10 99 5.961E-9
iee 10 4 dc 15.16E-6
hlim 90 0 vlim 1K
q1 11 2 13 qx
q2 12 1 14 qx
r2 6 9 100.0E3
rc1 3 11 5.305E3
rc2 3 12 5.305E3
re1 13 10 1.836E3
re2 14 10 1.836E3
ree 10 99 13.19E6
ro1 8 5 50
ro2 7 99 100
rp 3 4 18.16E3
vb 9 0 dc 0
vc 3 53 dc 1
ve 54 4 dc 1
vlim 7 8 dc 0
vlp 91 0 dc 40
vln 0 92 dc 40
.model dx D(Is=800.0E-18 Rs=1)
.model qx NPN(Is=800.0E-18 Bf=93.75)
.ends

```


```


vcm 1 0 0
vi1 2 1 sin(0 250m 2k 0 0)
vi2 1 4 sin(0 250m 2k 0 0)
x3 2 3 6 7 8 ua741
x2 4 5 9 10 11 ua741
r10 3 5 2.21k
r5 5 11 10k
vcc31 6 0 +15v
vcc32 7 0 -15v
vcc21 9 0 +15v
vcc22 10 0 -15v
r6 3 8 10k
r1 8 12 10k
r2 12 13 10k
r3 11 14 10k
r4 14 15 10k
vref 15 0 0
x1 14 12 16 17 13 ua741
vcc11 16 0 15v
vcc12 17 0 -15v
.tran 0.1u 10m
.control
run
plot v(2)-v(4)
plot v(13)
.endc
.end

```

3.2 Simulation Results


photodiode-amplifier

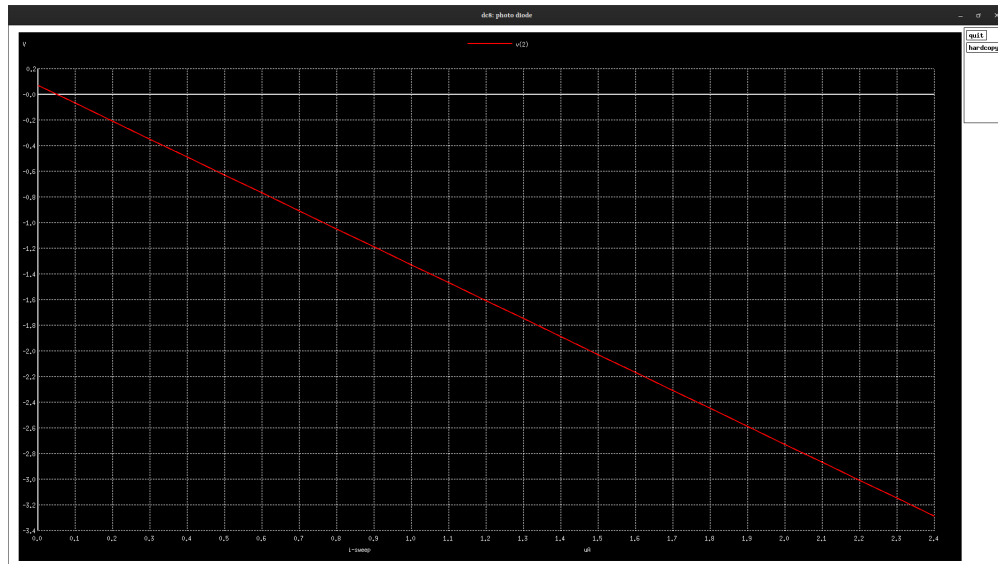


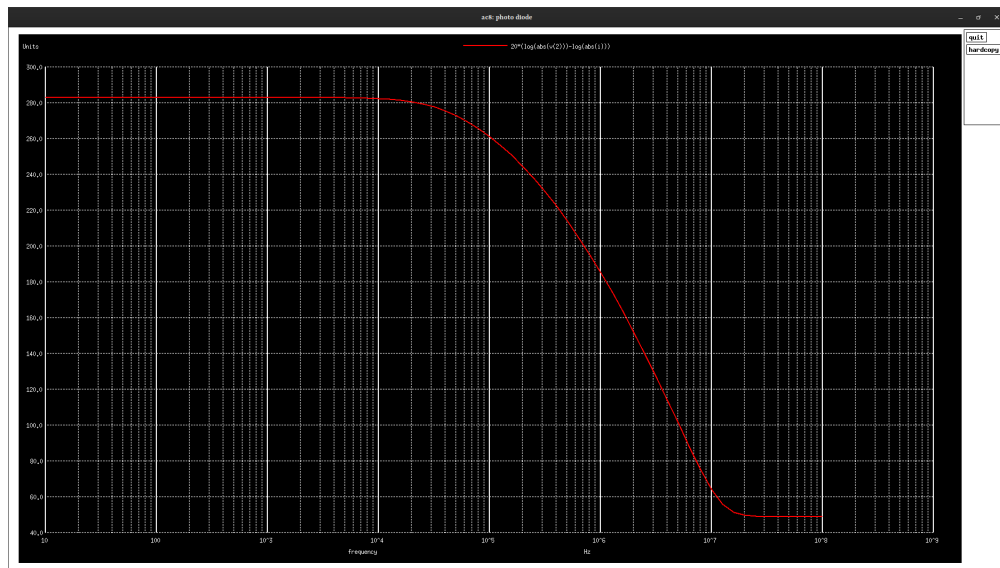



The cutoff frequency for the amplifier has been calculated using the 3dB frequency. Experimentally it came out to 580Hz

3 op-amp based Instrumentation Amplifier

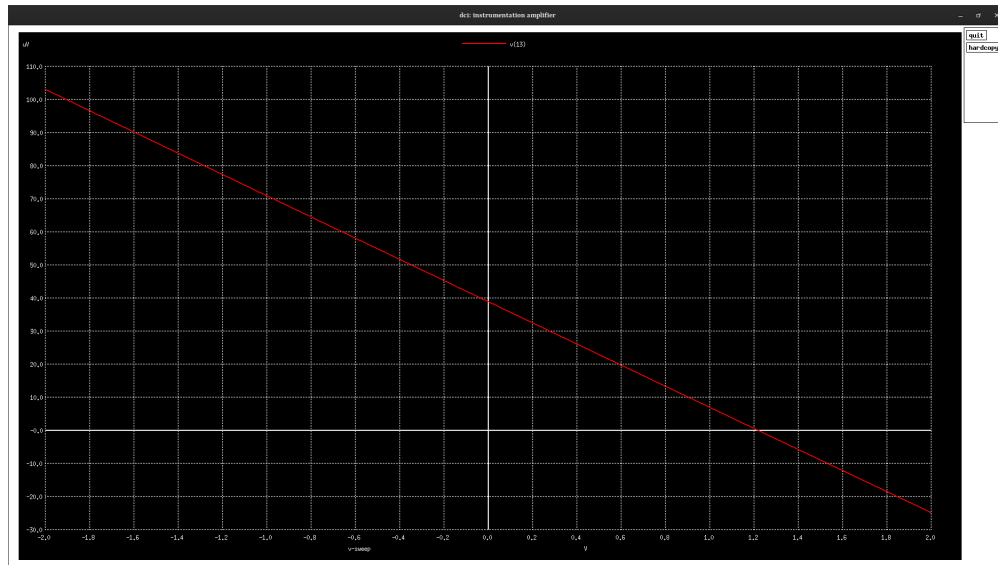

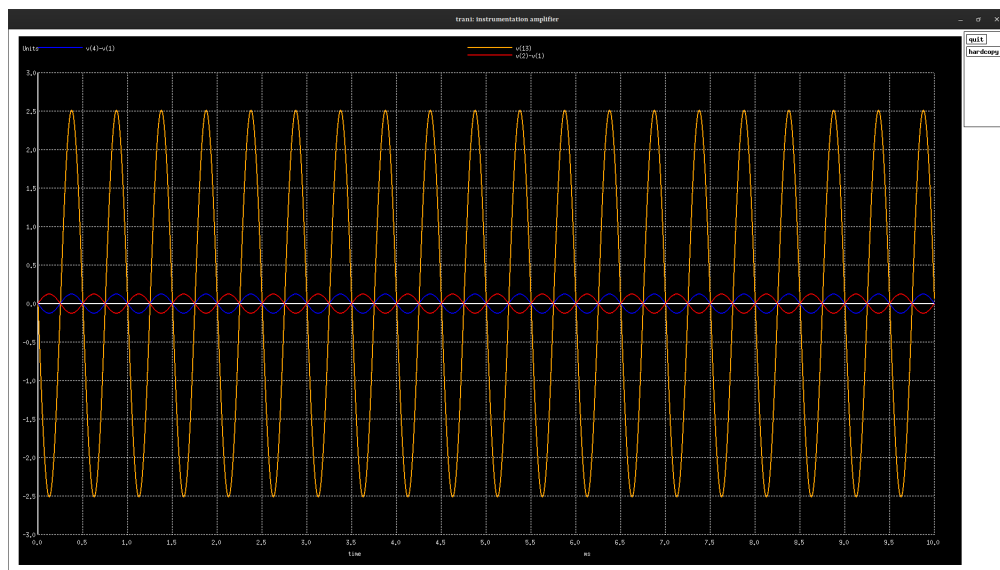

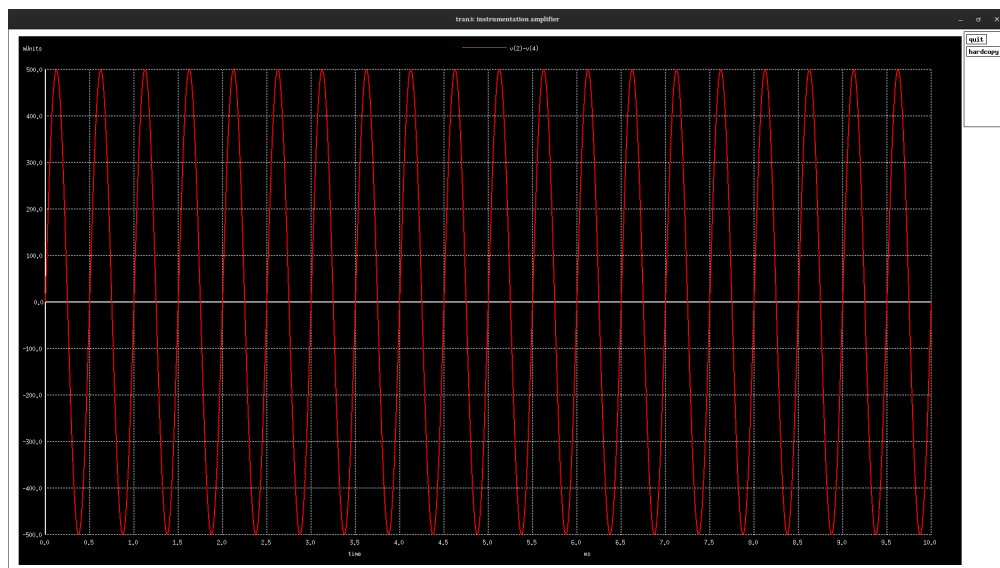

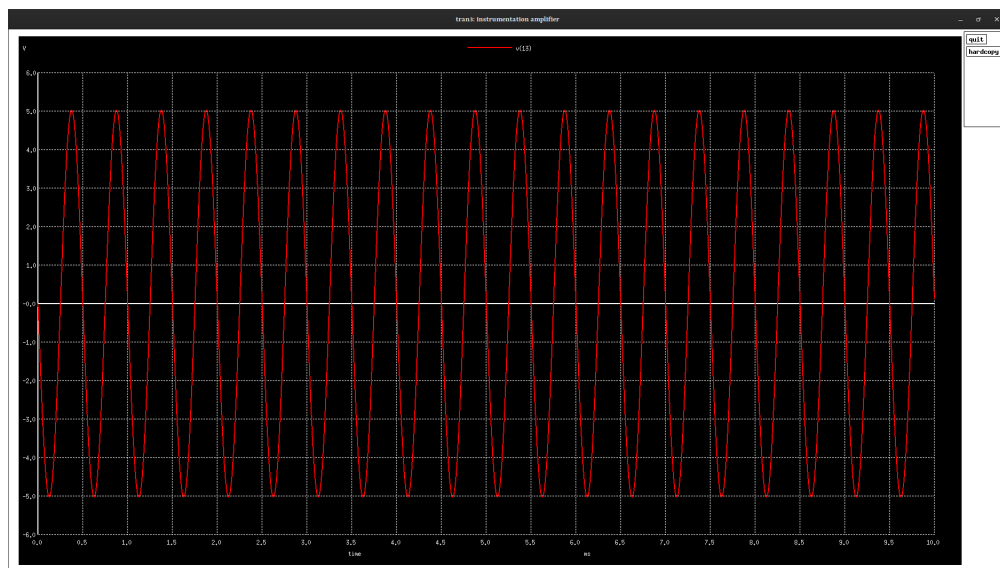

3.3 Explanation

$$gain = \frac{R4}{R3} * (1 + \frac{2R5}{R10}) \quad (1)$$

differential gain came out to be 10.