

# EE230:experiment No.6

## Non-idealities of opamp measurement

Mudavtah vishnuvardhan,200070044

March 6, 2022


## **1 Overview of the experiment**

### **1.1 Aim of the experiment**

- 1.To measure offset voltage of a non ideal opamp
- 2.To measure bias currents and offset current of non-ideal opamp
- 3.Measurement of DC open loop gain  $A_{ol}$

## 1.2 Method
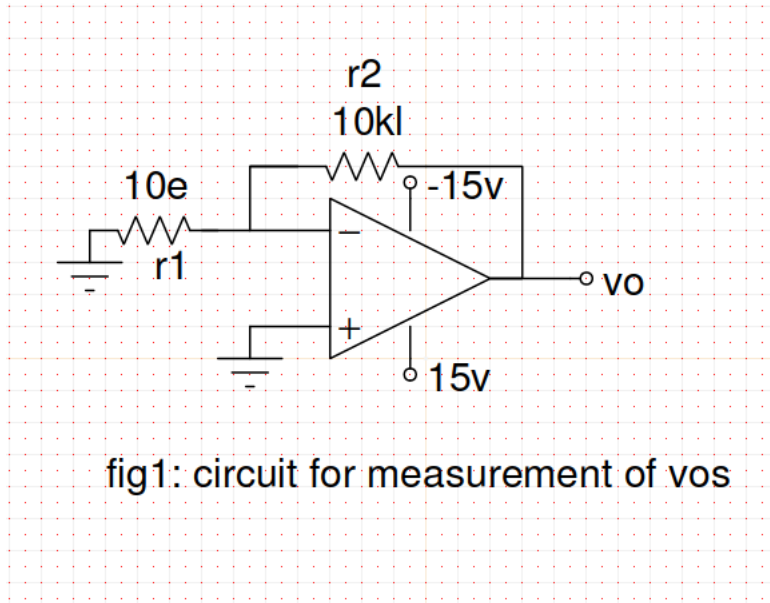
### 1.2.1 measurement of offset voltage ( $V_{os}$ )



circuit is connected as shown in figure , now for measurement of  $v_{os}$  we use this formula :

$$v_{os} = V_0 / (1 + R_2 / R_1)$$

For measurement we have done we got values for  $V_0$  as  $1.09v$ , thus

$$v_{os} = 1.08v / (1 + 10k / 10) = 1.09mv$$

In the datasheet ,typical value= $1mv$  and max possible value= $5mv$  and hence we can say that our possible value is correct.

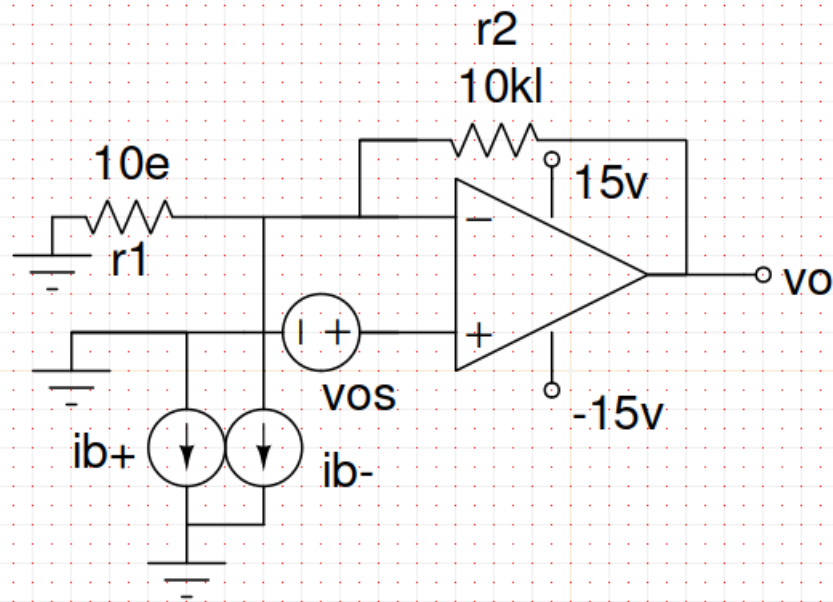


fig2: equivalent circuit

### 1.2.2 measurement of inverting bias current ( $I_{B-}$ )

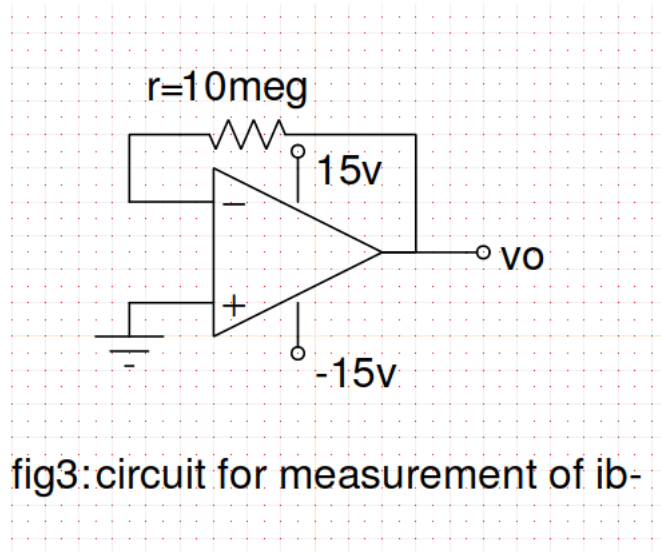


fig3:circuit for measurement of  $i_b$ -

circuit is connected as shown in figure , now for measurement of  $I_{B-}$  we use this formula :

$$I_{B-} = V_0/R$$

For measurement we have done we got values for  $V_0$  as  $3.37\text{v}$ ,thus

$$I_{B-} = 3.37/10^7 = 337\text{nA}$$


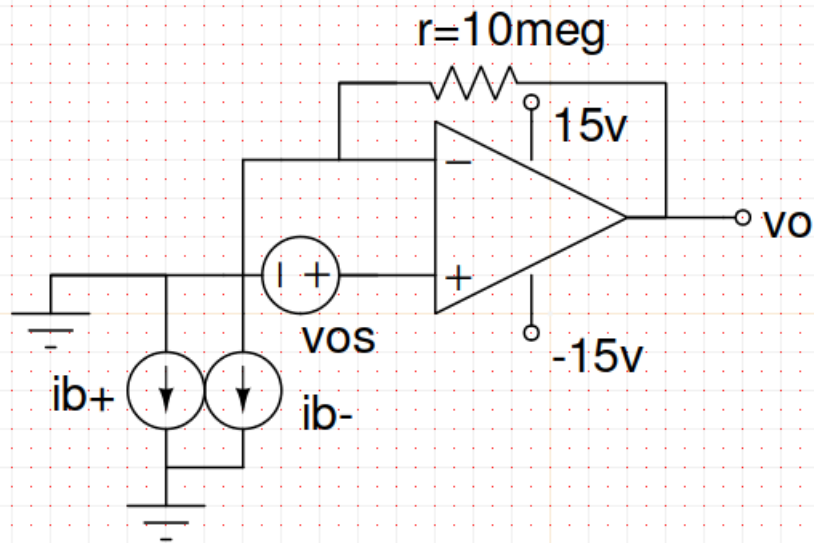


fig4: equivalent circuit for  $i_{b-}$  current measurement
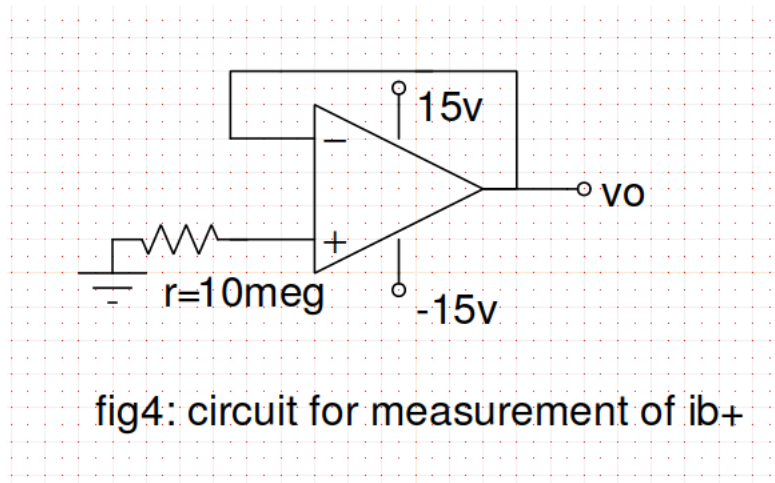
### 1.2.3 measurement of Non-inverting bias current ( $I_{B+}$ )



circuit is connected as shown in figure , now for measurement of  $I_{B+}$  we use this formula :

$$I_{B+} = V_0/R$$

For measurement we have done we got values for  $V_0$  as 3.92v,thus

$$I_{B-} = 3.92/10^7 = 392nA$$


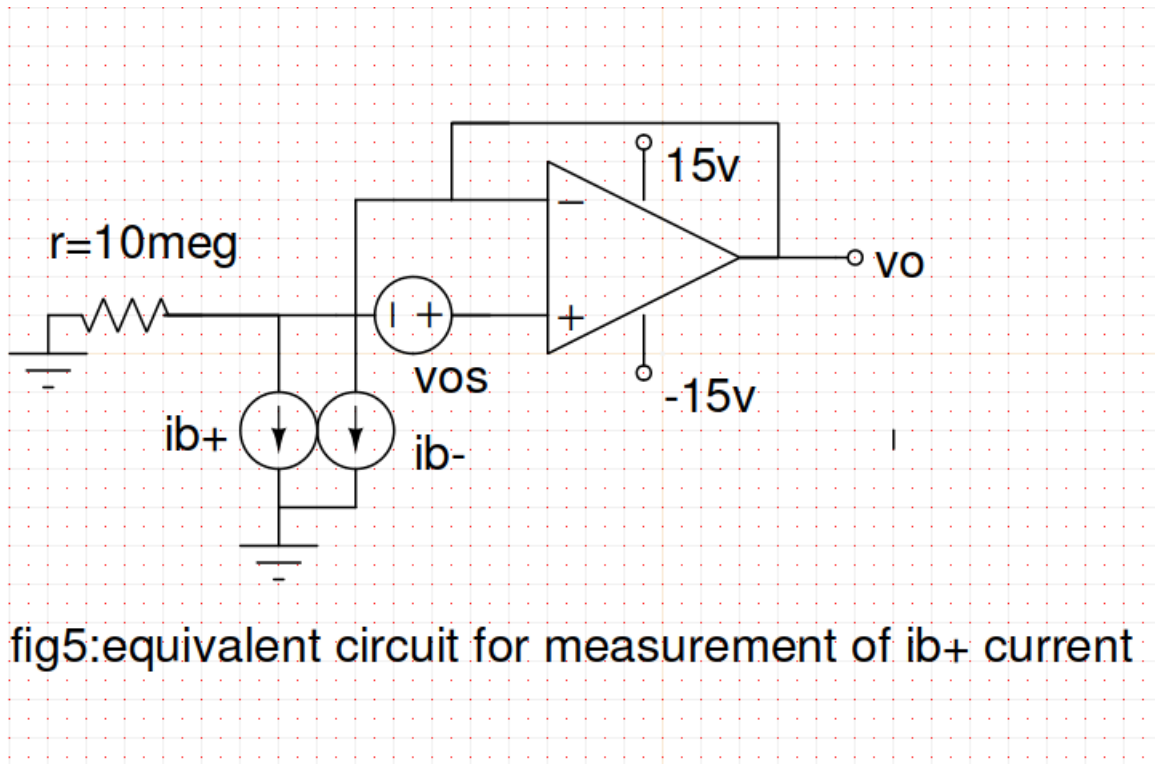


fig5:equivalent circuit for measurement of  $i_{b+}$  current

Typically these values are maximum 800nA as per the datasheet hence, we can conclude that our values match with datasheet.
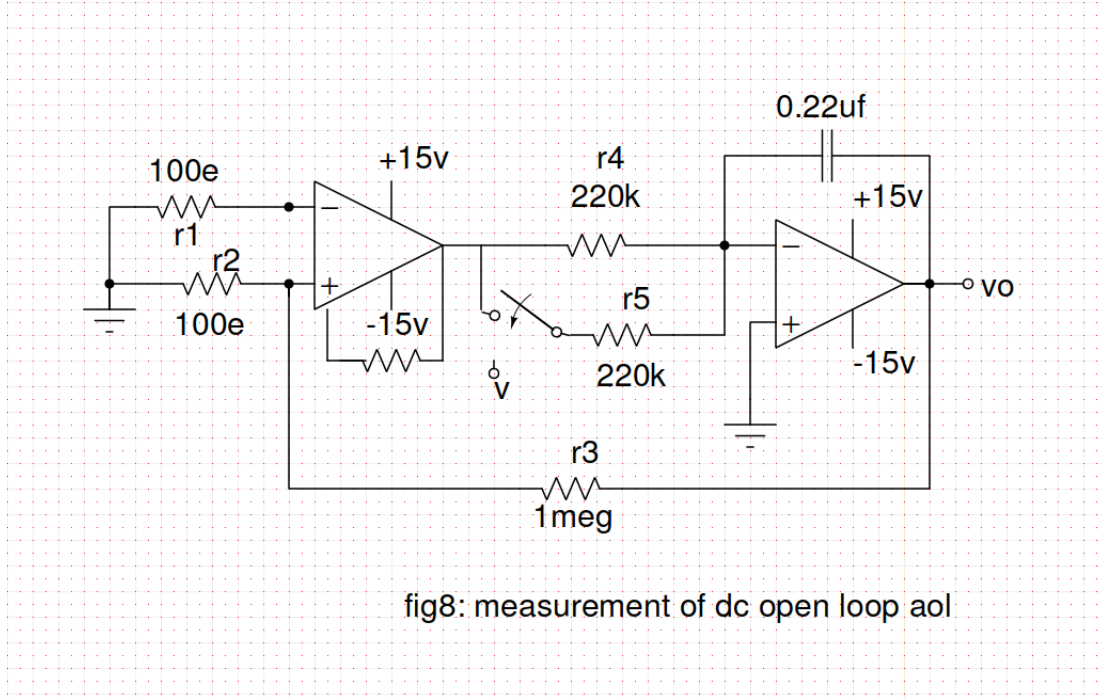
### 1.2.4 measurement of Open loop gain ( $A_{ol}$ )



circuit is connected as shown in figure , now for measurement of  $A_{ol}$  we use this formula :

$$A_{ol} = -V' * (R_2 + R_3 / R_2 * (V_{oB} - V_{oA}))$$

$V_{oB}$  and  $V_{oA}$  are values obtained when the circuit is in position 1 and 2 respectively.

**Values obtained for  $V' = 1v$ :**

$V_{oA} = 0.05v, V_{oB} = 0.01v$  which gives us  $A_{ol} = 2.5 * 10^5$ .

**Values obtained for  $V' = 2v$ :**

$V_{oA} = 0.05v, V_{oB} = -0.04v$  which gives us  $A_{ol} = 2.22 * 10^5$ .

**Values obtained for  $V' = 3v$ :**

$V_{oA} = 0.05v, V_{oB} = -0.1v$  which gives us  $A_{ol} = 2 * 10^5$ .

Theoretically,  $A_{ol} = 2 * 10^5$ , hence we can say our values almost match the actual values.



## **2 Experiment completion status**

I have completed all sections in Lab only.